LIGHTHOUSE

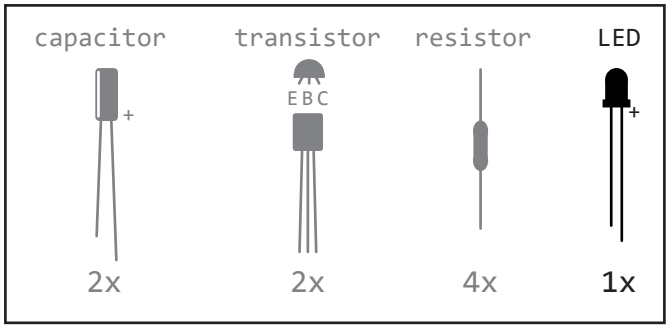

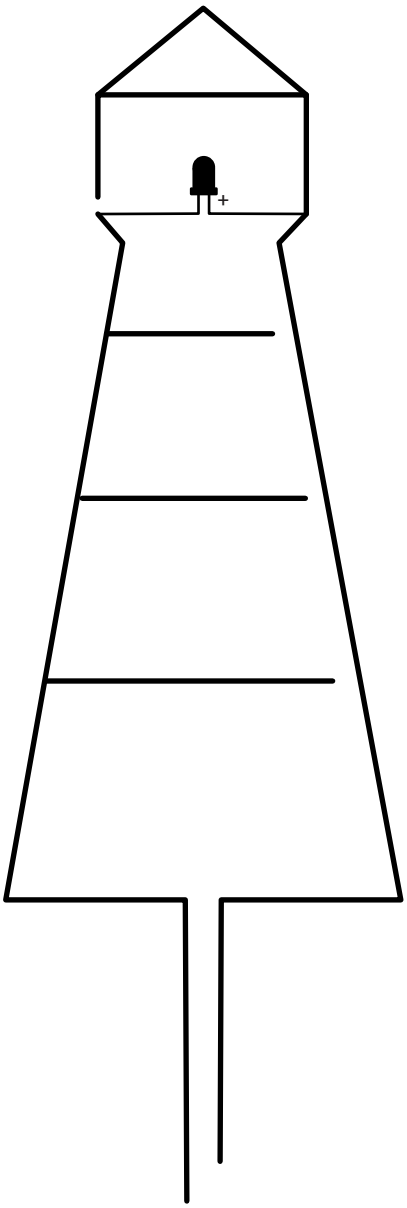

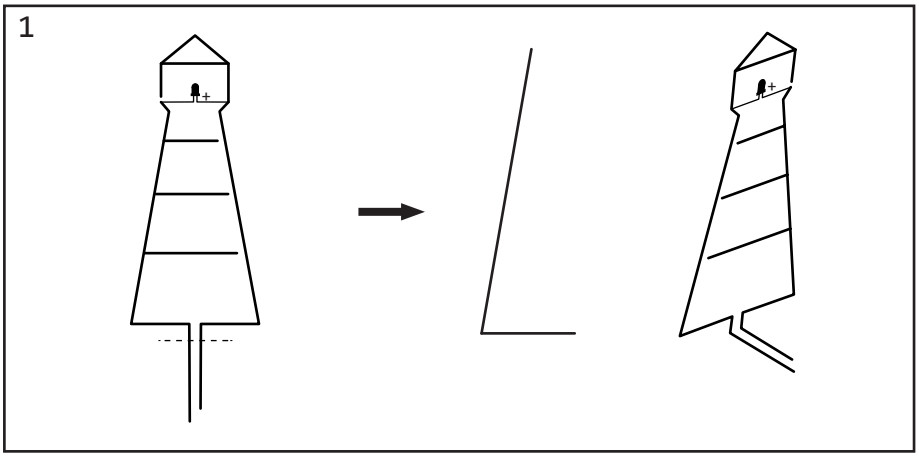

LIGHTHOUSE

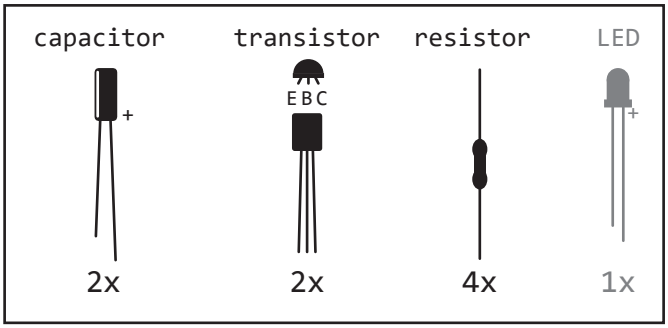
capacitor
transistor
resistor
LED
EBC
2x
2x
4x
1x

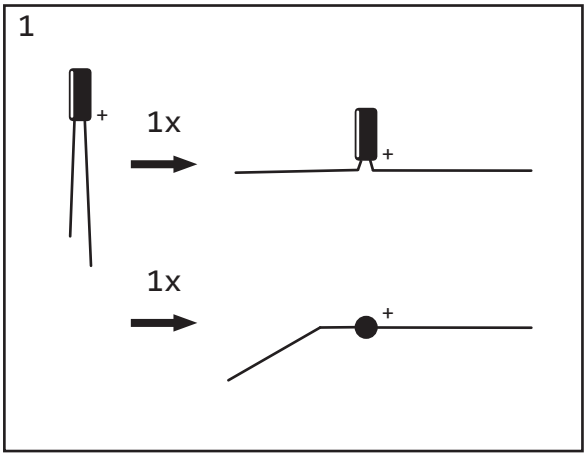
1
1x
1x

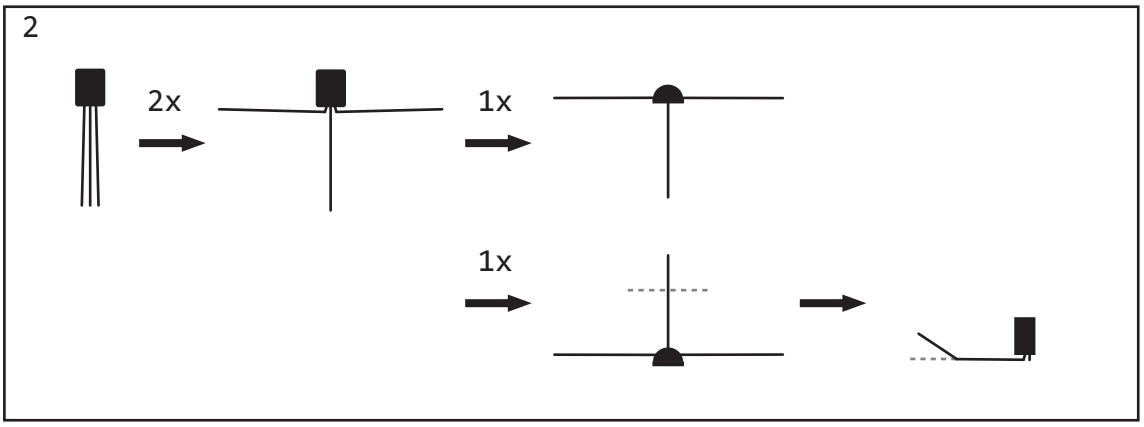
2
2x
1x
1x

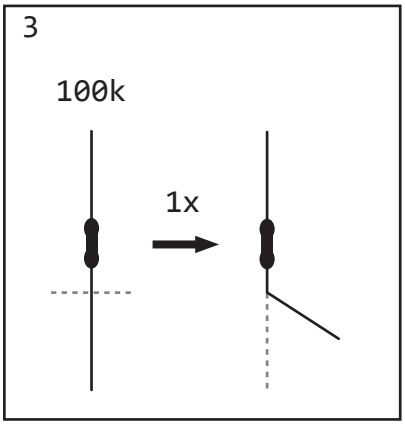
3
100k
1x

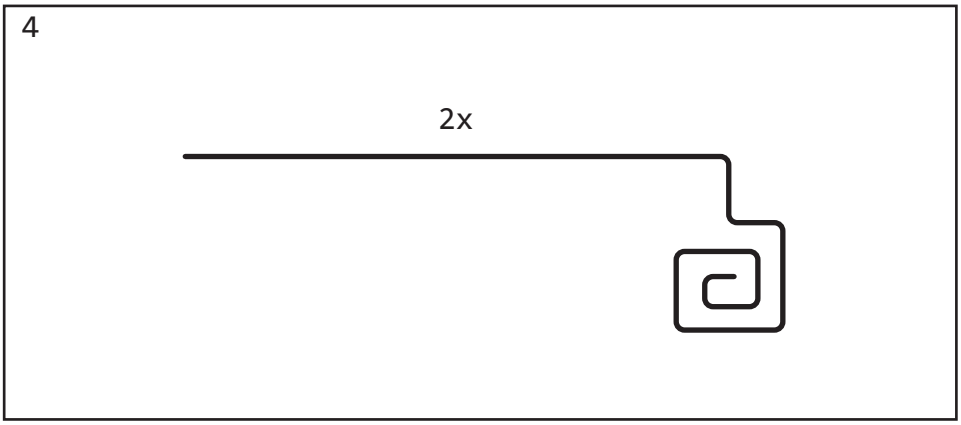
4
2x

LIGHTHOUSE

Place components here:

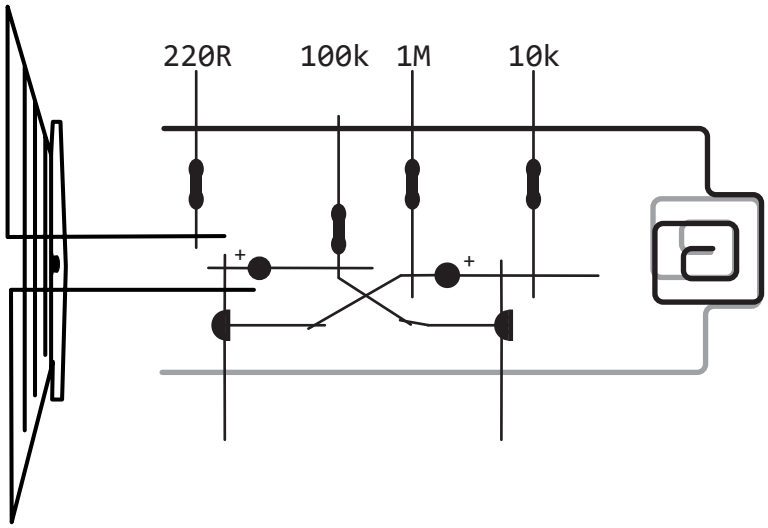

Follow these steps:

1 2x capacitor

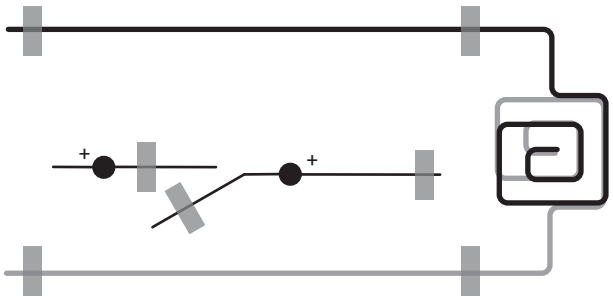

2 2x transistor

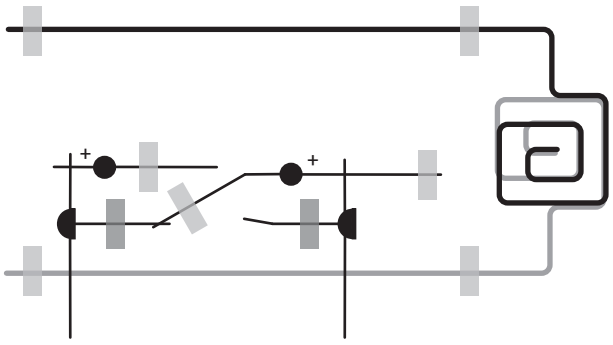

3 4x resistor

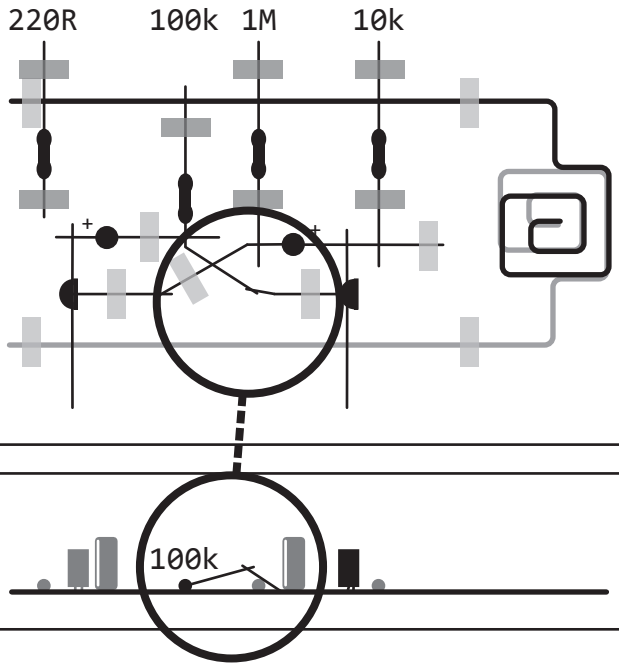

4

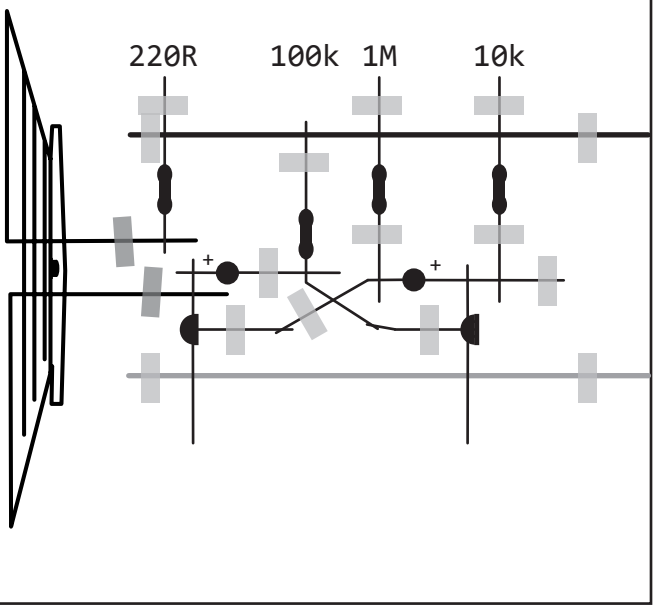

SCHEMATIC

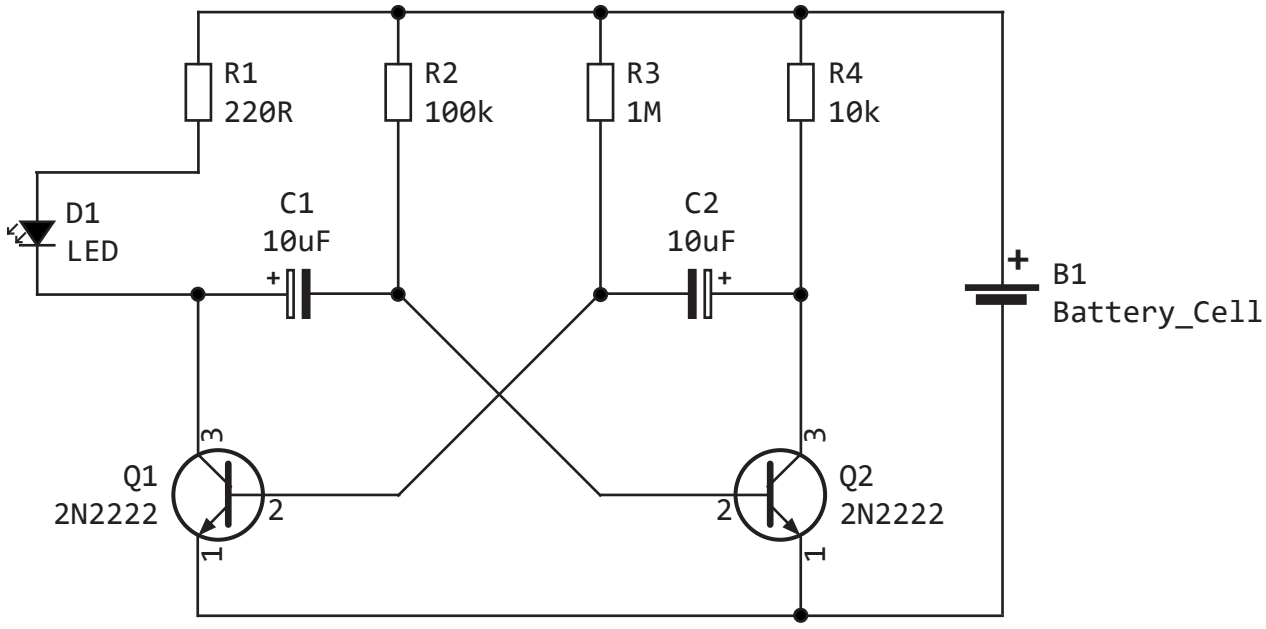
R1
220R
R2
100k
R3
1M
R4
10k
D1
LED
C1
10uF
C2
10uF
B1
Battery_Cell
Q1
2N2222
Q2
2N2222
1
2
3

4x 29cm

COMPONENTS

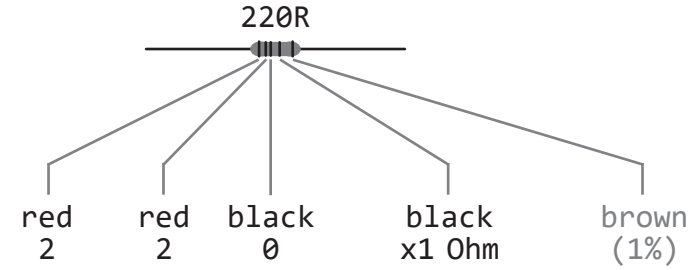

= 220 Ohm

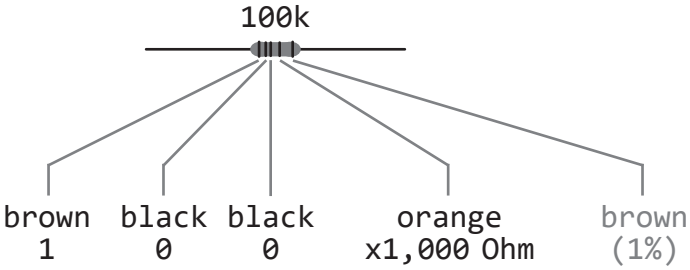

= 100,000 Ohm

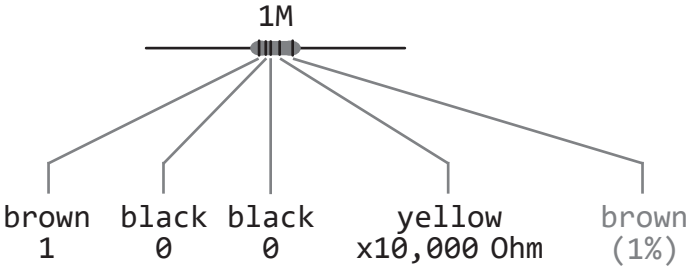

= 1,000,000 Ohm

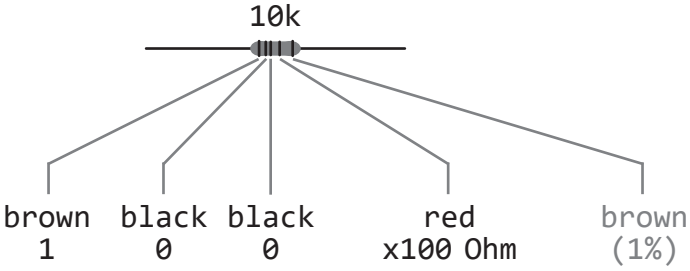
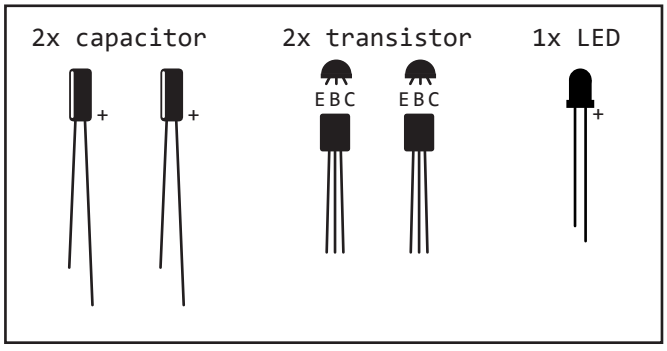
= 10,000 Ohm